

Homework 2

NYCU EE 112511210 黃仲璿

Introduction to Library: CIC 0.18um 1.8V/3.3V 1P6M virtual Mixed Mode/RFCMOS Process

Available corners: (pmos-nmos)

- TT (typical typical)
- FF (fast fast)
- SS (slow slow)
- FS
- SF

Available MOS Models

- N_18 (1.8v nmos)
- N_BPW_18 (1.8v p-well nmos)
- P_18 (1.8v pmos)
- N_33 (3.3v nmos)
- N_BPW_33
- P_33
- N_LV_18 (low threshold voltage 1.8v nmos)
- P_LV_18
- N_LV_33
- P_LV_33
- N_ZERO_18 (zero Vt 1.8v nmos)
- N_ZERO_33

Design Rule

```
****Layout-Dependent Parasitics Model Parameters****
+   LMIN = 1.8000E-07   LMAX = 5.0000E-05
+   WMIN = 2.5000E-07   WMAX = 1.0000E-04
```

Library Summary

For homework simulation, use:

- TT type
- N_18 and P_18 for 1.8V nmos and pmos
- LMIN = 0.18u and WMIN = 0.25u
- assume minimal channel length/width delta = 0.01u
- assume temperature = 27 C

Problem 2-1-1

Initial Guess

Source Code

```
* HW2_1_1.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post

*-----
* Simulation netlist
*-----
Vd d gnd 0.9
Vg g gnd 0.9
Vdd ndd gnd 1.8

MN1 d g gnd gnd N_18 W=0.25u L=0.18u
MP1 d g ndd ndd P_18 W=0.25u L=0.18u

*-----
* Stimulus
*-----
.op
.end
```

Simulation Result

```
...
element 0:mn1      0:mp1
model    0:n_18.1  0:p_18.1
region   Saturati  Saturati
id        45.7379u -10.5697u
...
```

We see that **id** of nmos is 4.5 times larger than target (10u), and **id** of pmos is very close to target (10u).

Note:

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

pmos: fine-tune **Lp** up one step (0.01u) every time. nmos: change **Ln** to 4.5 times the original (0.81u), then perform fine-tuning.

NMOS Tuning

Source Code

```
* HW2_1_1_b.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post

*-----
* Simulation netlist
*-----
*nmos
Vg g gnd 0.9
Vd d gnd 0.9
Vdd ndd gnd 1.8

MN1 d g gnd gnd N_18 W=0.25u L=LN
*MP1 d g ndd ndd P_18 W=0.25u L=LP

*MN1 d g gnd gnd N_18 W=0.25u L=0.18u
*MP1 d g ndd ndd P_18 W=0.25u L=0.18u

*-----
* Stimulus
*-----

.dc Vdd 0 1.8 1.8 sweep LN 0.81u 1.0u 0.01u
*.dc Vg 0 0.9 0.9 sweep LP 0.18u 0.2u 0.01u

.probe i1(MN1)
*.probe i1(MP1)
.meas DC IMeas find i1(MN1) when v(g)=0.9
*.meas DC IMeas find i1(MP1) when v(g)=0.9
.end
```

Simulation Result:

```
...
*****
* hw2_1_1_b.sp
*** parameter ln = 900.0000n ***
imeas= 1.0025E-05
*****
```

```
* hw2_1_1_b.sp
*** parameter ln = 910.0000n      ***
imeas= 9.9322E-06
*****
...
```

when Ln parameter $ln = 0.9u$, id is closest to 10uA (1.0025E-05 A).

PMOS Tuning

Source Code: same as above except tune pmos

Simulation Result:

```
...
*****
* hw2_1_1_b.sp
*** parameter lp = 180.0000n      ***
imeas= -1.0570E-05
*****

* hw2_1_1_b.sp
*** parameter lp = 190.0000n      ***
imeas= -9.2225E-06
*****
...
```

when Lp parameter $lp = 0.18u$, id is closest to 10uA (-1.0570E-05 A)

Result

For nmos we choose $Wn = 0.25u$, $Ln = 0.9u$.

For pmos we choose $Wp = 0.25u$, $Lp = 0.18u$.

Problem 2-1-2

NMOS

```
* HW2_1_2.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post

*-----
* Simulation netlist
*-----
Vg g gnd 0.9
```

```


Vd d gnd 0.9
Vdd nnd gnd 1.8

MN1 d g gnd gnd N_18 W=0.25u L=0.9u

*-----
* Stimulus
*-----

.dc Vd 0 1.8 0.01 sweep Vg 0.7 1.0 0.1
.probe i1(MN1)

```

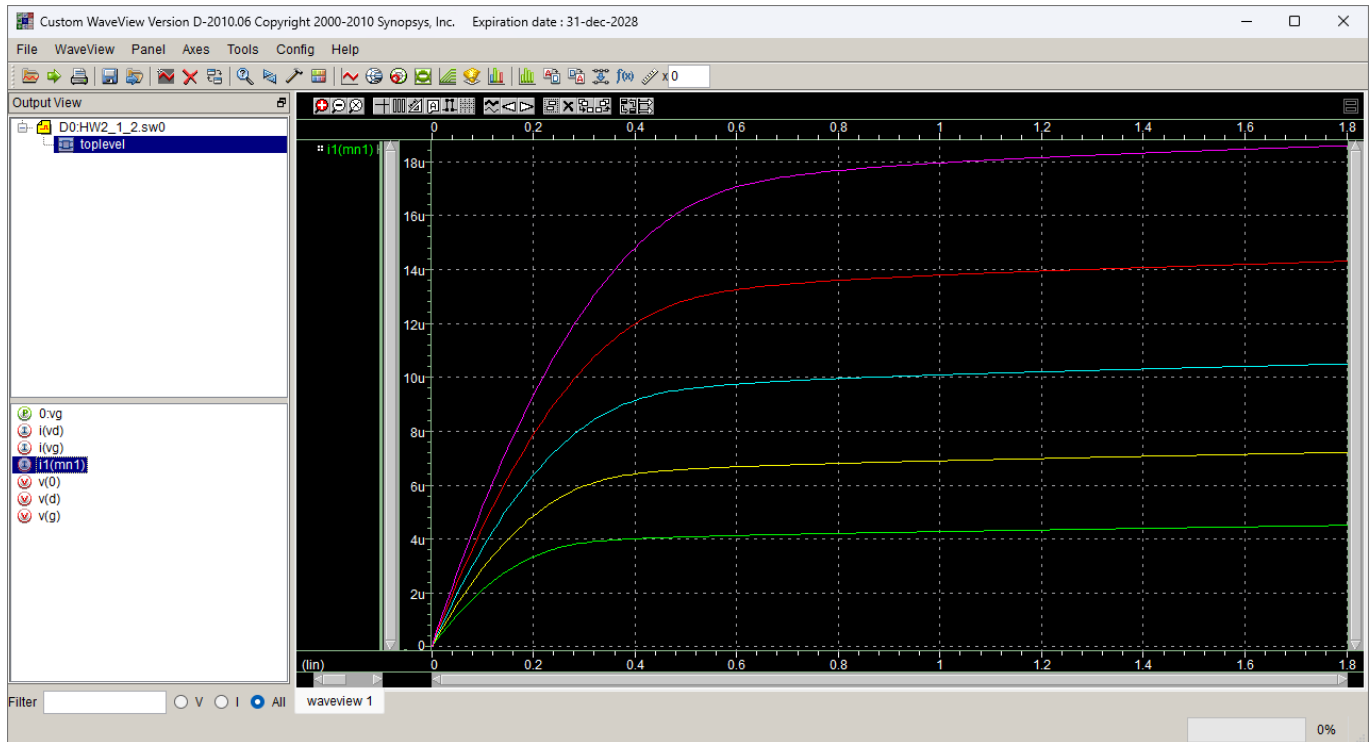

PMOS

```

* HW2_1_2.sp
*-----

.lib 'cic018.1' tt
.temp 27
.option post

```

```

*-----
* Simulation netlist
*-----

```

```

Vg g gnd 0.9
Vd d gnd 0.9
Vdd nnd gnd 1.8

```

```

MP1 d g nnd nnd P_18 W=0.25u L=0.18u


```

```

*-----
* Stimulus
*-----

```

```
.dc Vd 0 1.8 0.01 sweep Vg 0.7 1.0 0.1
.probe i1(MP1)
```

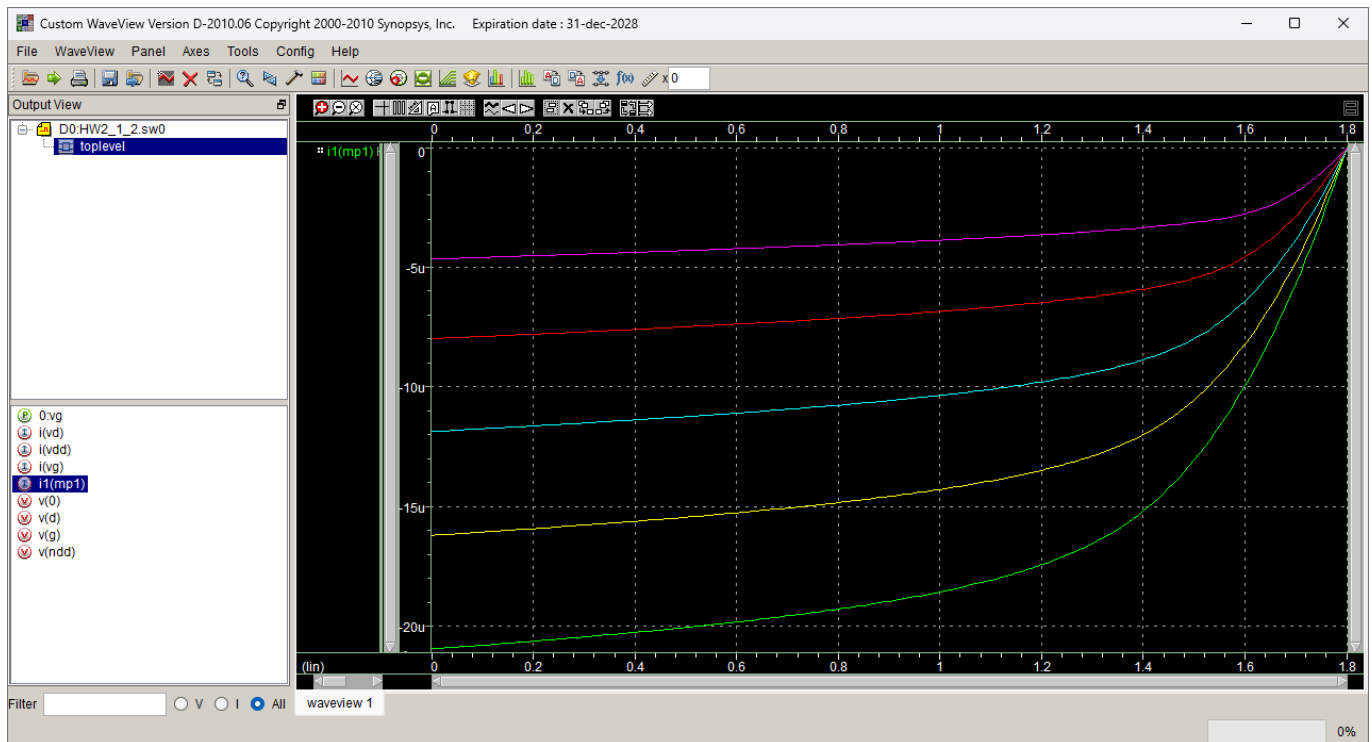

Problem 2-2-1

Parallel connecting M nmoses is the equivalent of multiplying I_n by M, thus multiplying I_o . The same idea applies to pmos. Therefore, to have $I_o = 10\mu A$, $20\mu A$, $30\mu A$, we use:

```
*Io = 10u
MN1 d g gnd gnd N_18 W=0.25u L= 0.9u M=1
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=1

*Io = 20u
MN1 d g gnd gnd N_18 W=0.25u L= 0.9u M=2
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=2

*Io = 30u
MN1 d g gnd gnd N_18 W=0.25u L= 0.9u M=3
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=3
```

$I_o = 10\mu A$ ($M = 1$)

```
* HW2_2_1.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post
```

```

*-----
* Simulation netlist
*-----


Vg g gnd
Vdd ndd gnd 1.8

MN1 d g gnd gnd N_18 W=0.25u L=0.90u M=1
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=1

*-----
* Stimulus
*-----

.dc Vg 0 1.8 0.01
.probe i1(MN1)
.end

```

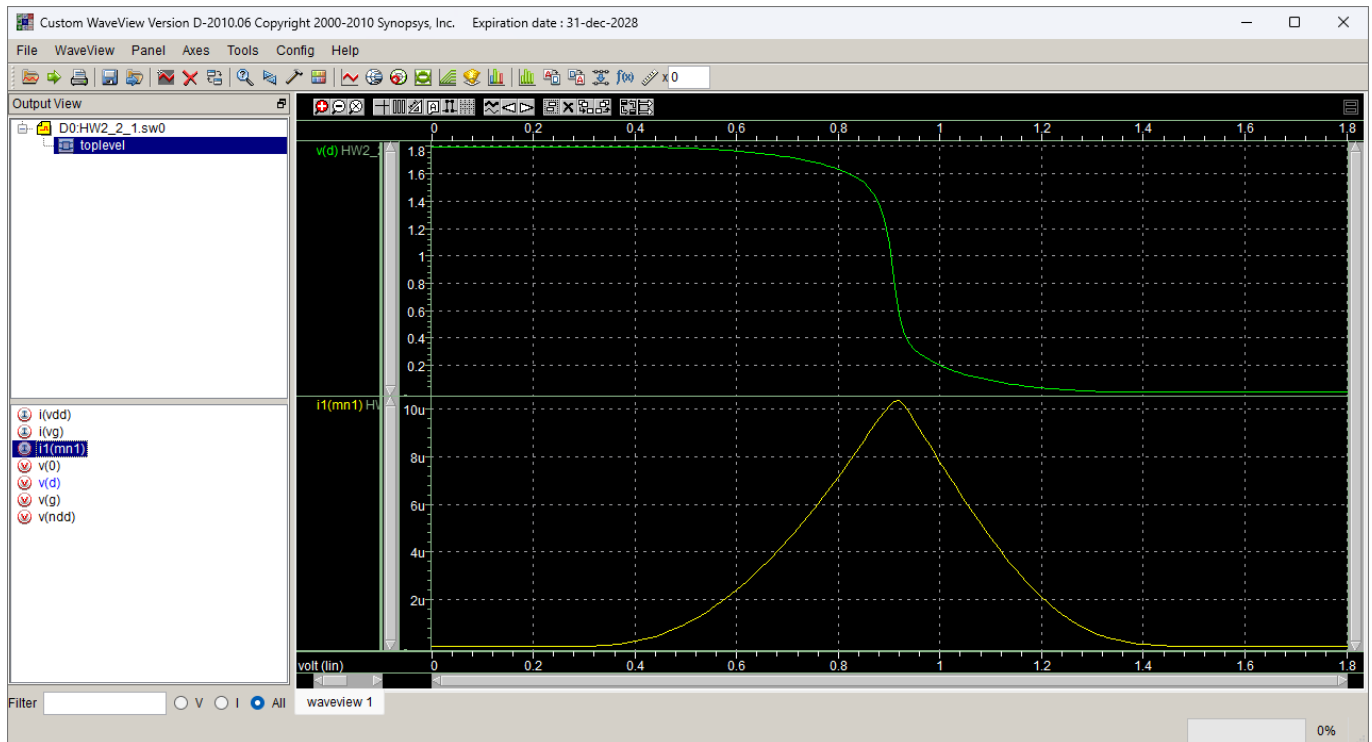


$I_o = 20\mu A$ ($M = 2$)

Code same as above, except

```

MN1 d g gnd gnd N_18 W=0.25u L=0.90u M=2
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=2

```

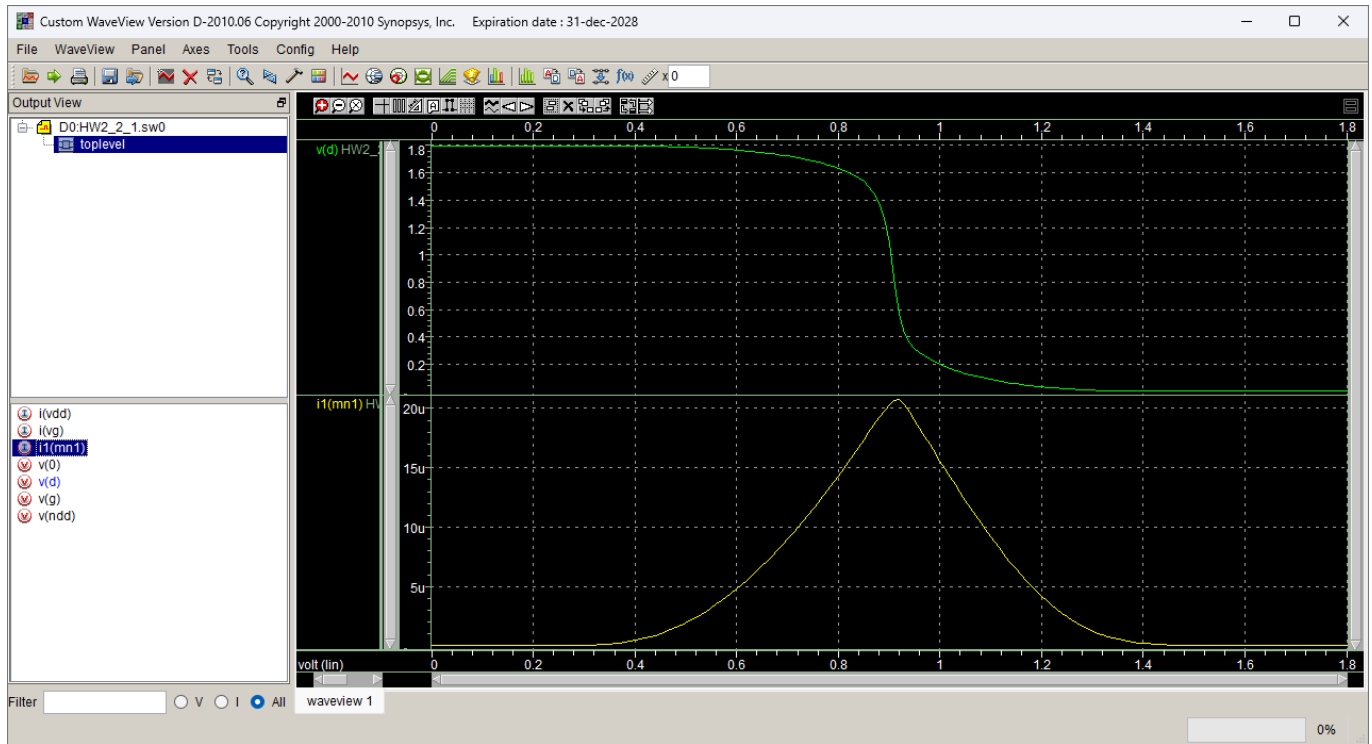


$I_o = 30\mu A$ ($M = 3$)

Code same as above, except

```

MN1 d g gnd gnd N_18 W=0.25u L=0.90u M=3
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=3

```

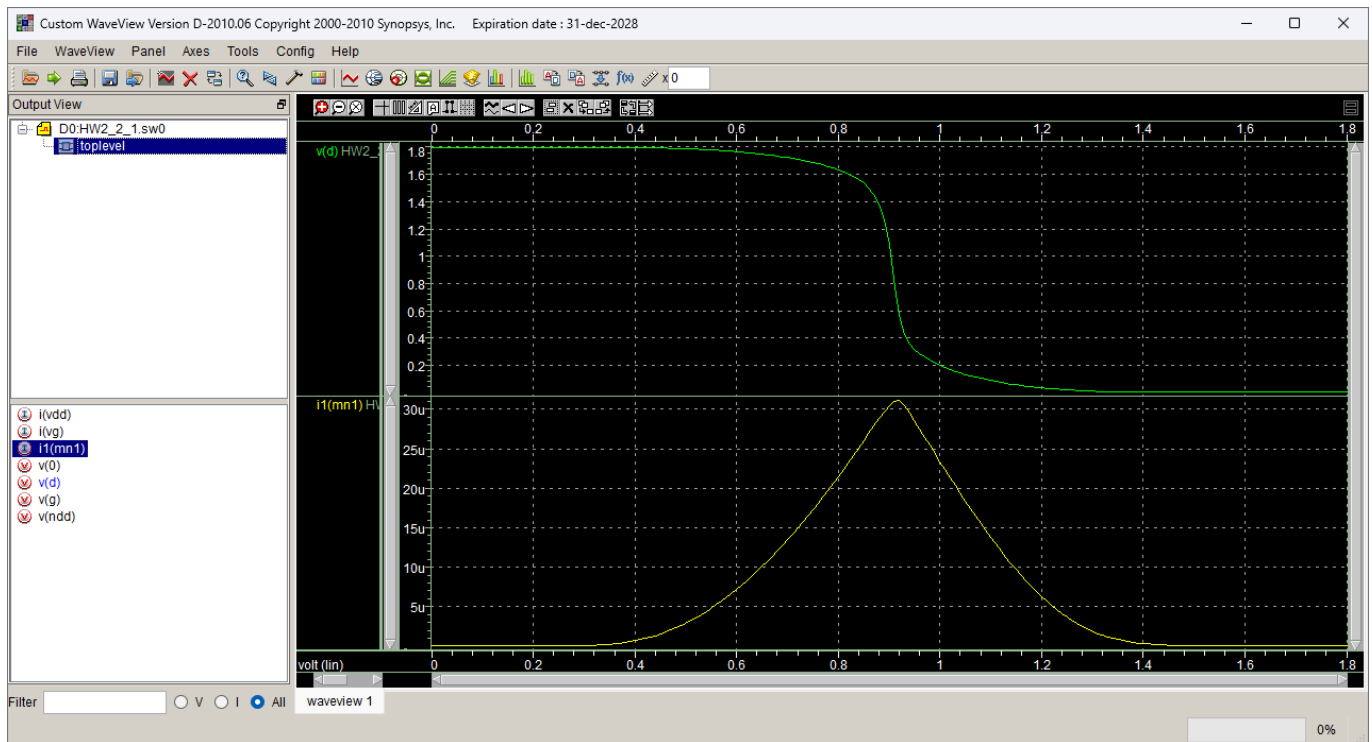

Problem 2-2-2

$$V_1 = 0.7V$$

Initial Guess

Source Code: same as Problem 2-1-1 except set all V_g to 0.7

Simulation Result:

```

element  0:mn1      0:mp1
model    0:n_18.1   0:p_18.1
region   Saturati   Saturati
id       21.5095u   -18.9496u

```

We see that i_d of both nmos and pmos are very close to target (20u).

- pmos: to increase current, fine-tune W_p up one step (0.01u) every time.
- nmos: to decrease current, fine-tune L_n up one step (0.01u) every time.

NMOS

Simulation Result:

```

...
* hw2_2_2_07.sp
*** parameter ln = 180.0000n      ***
imeas= 2.1509E-05
*****
* hw2_2_2_07.sp
*** parameter ln = 190.0000n      ***
imeas= 1.9373E-05
...

```

when L_n parameter $ln = 0.19u$, i_d is closest to 20uA (1.9373E-05 A)

PMOS

Simulation Result:

```

...
* hw2_2_2_07.sp
*** parameter wp = 260.0000n      ***
1.80000      -19.9722u
*****
* hw2_2_2_07.sp
*** parameter wp = 270.0000n      ***
1.80000      -20.9425u
...

```

when Wp parameter $w_p = 0.26\mu$, id is closest to 20uA (-19.9722u A)

Result

nmos W = 0.25u L = 0.19u

pmos W = 0.26u L = 0.18u


```
* HW2_2_2_07_dc.sp
*-----
.lib 'cic018.l' tt
.temp 27
.option post

*-----
* Simulation netlist
*-----
Vg g gnd
*Vd d gnd 0.9
Vdd ndd gnd 1.8

MN1 d g gnd gnd N_18 W=0.25u L=0.19u
MP1 d g ndd ndd P_18 W=0.26u L=0.18u

*-----
* Stimulus
*-----

.dc Vg 0 1.8 0.01
.op
.end
```

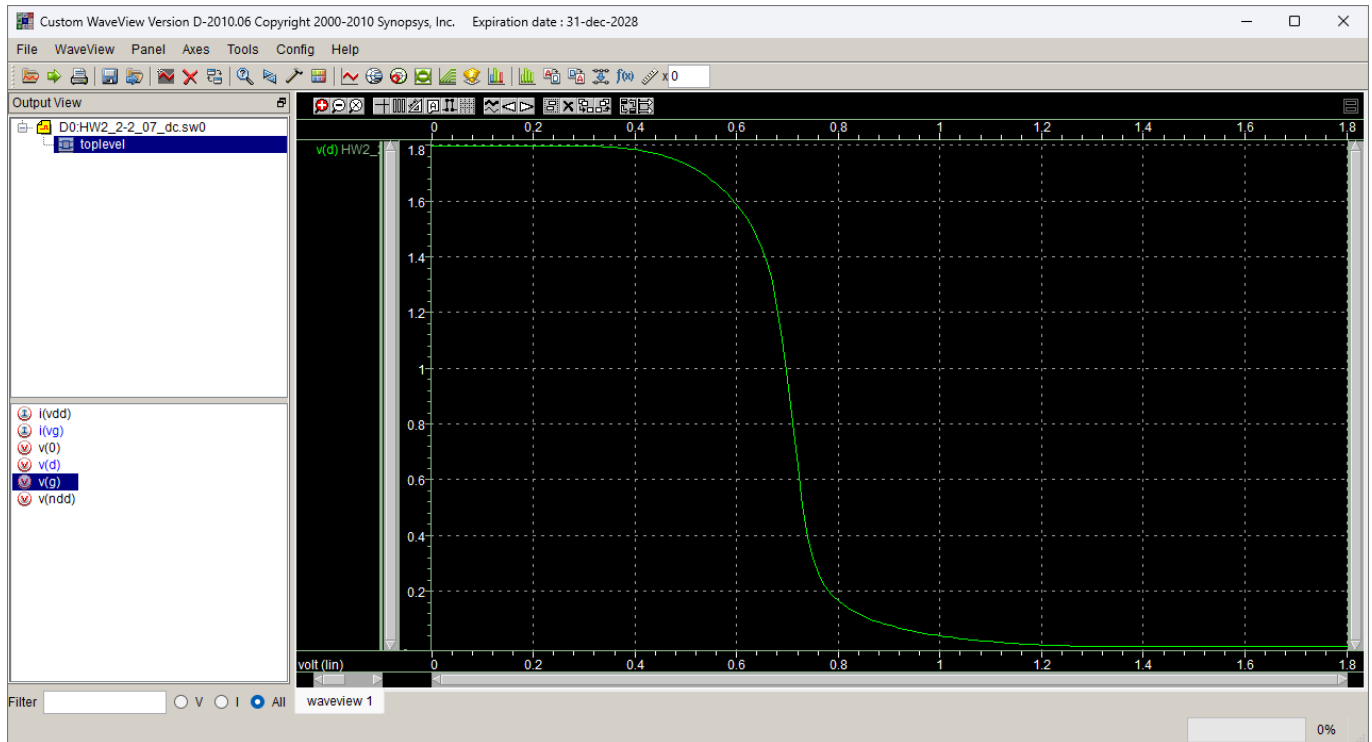

$$V_g = 0.8$$

Initial Guess

Source Code: same as Problem 2-1-1 except set all V_g to 0.8

Simulation Result:

```

element  0:mn1      0:mp1
model    0:n_18.1   0:p_18.1
region    Saturati  Saturati
id        33.1641u  -14.5751u

```

We see that i_d of both nmos and pmos are very close to target (20u).

- pmos: to increase current, fine-tune W_p up one step (0.01u) every time.
- nmos: to decrease current, multiply L_n by 1.2 (0.22u), then fine-tune L_n up one step (0.01u) every time.

NMOS

```

* hw2_2_2_08.sp
*** parameter ln = 260.0000n ***
imeas= 2.0368E-05
*****
* hw2_2_2_08.sp
*** parameter ln = 270.0000n ***
imeas= 1.9564E-05

```

when L_n parameter $l_n = 0.29\mu$, i_d is closest to $20\mu A$ ($2.0368E-05 A$)

PMOS

```
* hw2_2_2_08.sp
*** parameter wp = 330.0000n      ***
    1.80000      -19.9570u
*****
* hw2_2_2_08.sp
*** parameter wp = 340.0000n      ***
    1.80000      -20.5651u
```

when W_p parameter $w_p = 0.33\mu$, i_d is closest to $20\mu A$ ($-19.9570\mu A$)

Result

nmos $W = 0.25\mu$ $L = 0.29\mu$

pmos $W = 0.33\mu$ $L = 0.18\mu$

```
* HW2_2_2_08_dc.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post

*-----
* Simulation netlist
*-----
Vg g gnd
*Vd d gnd 0.9
Vdd ndd gnd 1.8

MN1 d g gnd gnd N_18 W=0.25u L=0.29u
MP1 d g ndd ndd P_18 W=0.33u L=0.18u

*-----
* Stimulus
*-----

.dc Vg 0 1.8 0.01
.op
.end
```


$V_g = 0.9$

Same as Problem 2-2-1 **nmos W = 0.25u L = 0.90u M = 2**

pmos W = 0.25u L = 0.18u M = 2


```
* HW2_2_1.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post
```

```
*-----
* Simulation netlist
*-----
```

```
Vg g gnd
Vdd ndd gnd 1.8
```

```
MN1 d g gnd gnd N_18 W=0.25u L=0.90u M=2
MP1 d g ndd ndd P_18 W=0.25u L=0.18u M=2
```
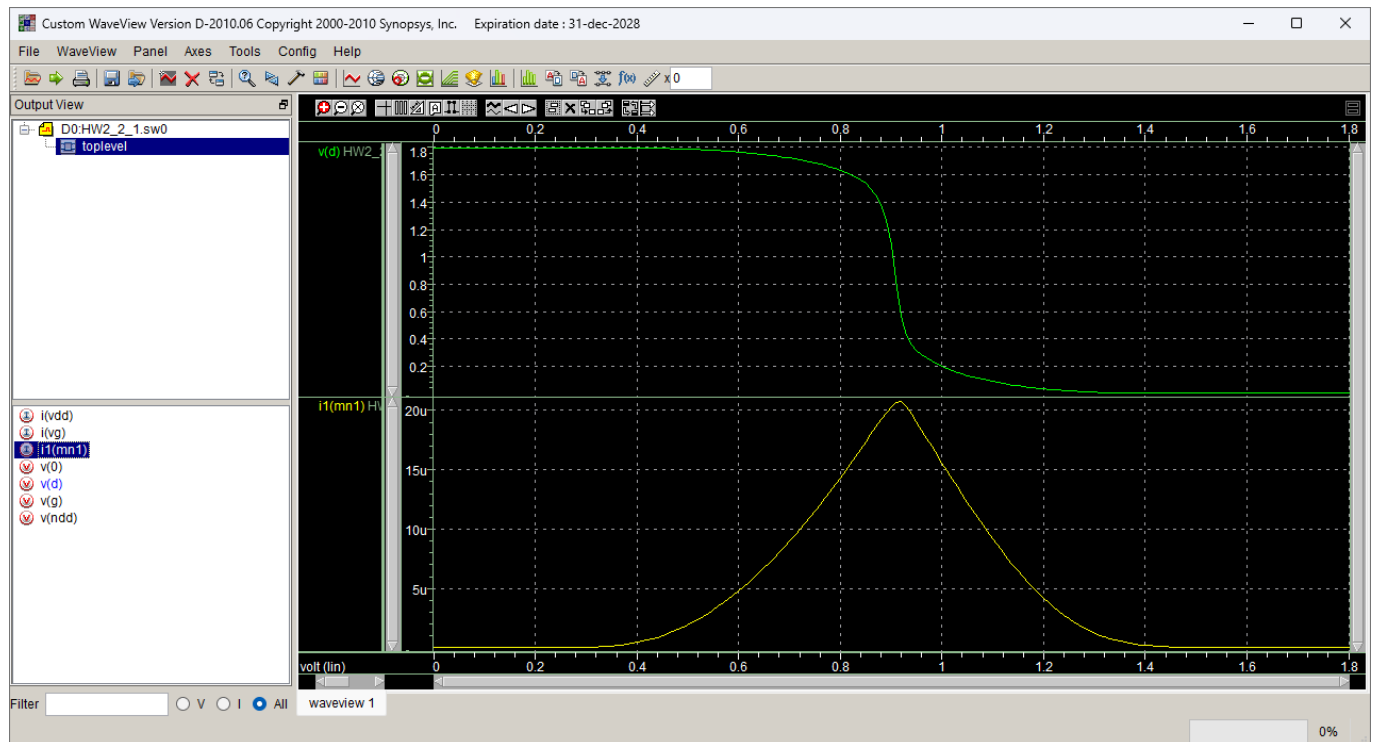
```
*-----
* Stimulus
*-----
.dc Vg 0 1.8 0.01
.probe i1(MN1)
.end
```



$V_g = 1.0$

Initial Guess

Source Code: same as Problem 2-1-1 except set all V_g to 1.0

Simulation Result:

```

element  0:mn1      0:mp1
model    0:n_18.1   0:p_18.1
region   Saturati   Saturati
id       60.0367u   -6.8436u

```

We see that **id** of nmos is roughly 3 times larger than the target (20uA), and pmos is roughly third of such.

- pmos: to increase current, multiply **Wp** by 2 (0.50u), fine-tune **Wp** up one step (0.01u) every time.
- nmos: to decrease current, multiply **Ln** by 3 (0.75u), then fine-tune **Ln** up one step (0.01u) every time.

NMOS

```

* hw2_2_2_10.sp
*** parameter ln = 570.0000n      ***
    1.80000      20.2303u
*****
* hw2_2_2_10.sp
*** parameter ln = 580.0000n      ***
    1.80000      19.9363u

```

when Ln parameter **ln** = 0.58u, id is closest to 20uA (19.9363u A)

PMOS

```

* hw2_2_2_10.sp
*** parameter wp = 790.0000n      ***
    1.80000      -19.8113u
*****
* hw2_2_2_10.sp
*** parameter wp = 800.0000n      ***
    1.80000      -20.0495u

```

when Wp parameter **wp** = 0.80u, id is closest to 20uA (-20.0495u A)

Result

nmos W = 0.25u L = 0.58u

pmos W = 0.80u L = 0.18u

```

* HW2_2_2_10_dc.sp
*-----
.lib 'cic018.1' tt
.temp 27

```

```
.option post
```

```
*-----
* Simulation netlist
*-----
```

```
Vg g gnd
```

```
*Vd d gnd 0.9
```

```
Vdd ndd gnd 1.8
```

```
MN1 d g gnd gnd N_18 W=0.25u L=0.58u
```


```
MP1 d g ndd ndd P_18 W=0.80u L=0.18u
```

```
*-----
* Stimulus
*-----
```

```
.dc Vg 0 1.8 0.01
```

```
.op
```

```
.end
```

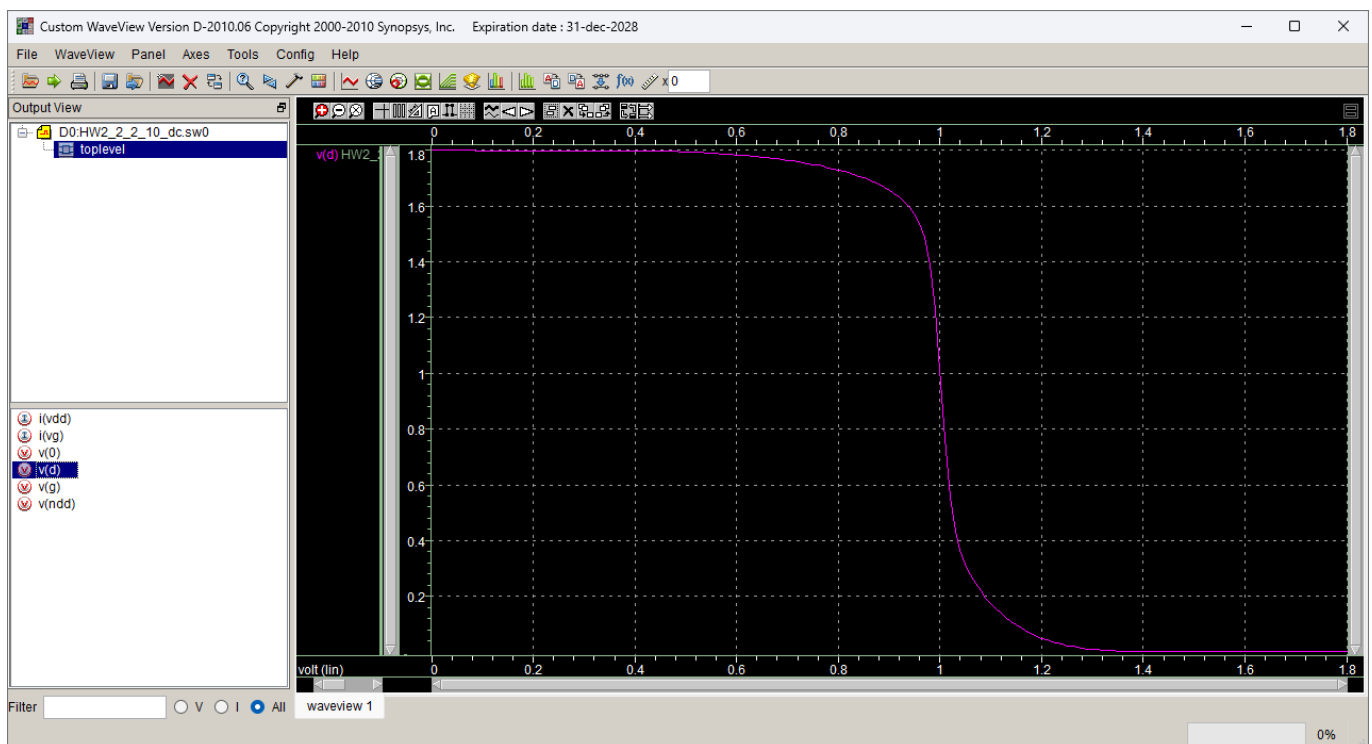

$$V_g = 1.1$$

Initial Guess

Source Code: same as Problem 2-1-1 except set all V_g to 1.1

Simulation Result:

```
element 0:mn1      0:mp1
model   0:n_18.1   0:p_18.1
```

region	Saturati	Saturati
id	73.6641u	-3.8705u

We see that **id** of nmos is roughly 3.5 times larger than the target (20uA), and pmos is roughly sixth of such.

- pmos: to increase current, multiply **Wp** by 5 (1.25), fine-tune **Wp** up one step (0.01u) every time.
- nmos: to decrease current, multiply **Ln** by 6 (0.84u), then fine-tune **Ln** up one step (0.01u) every time.

NMOS

```
* hw2_2_2_11.sp
*** parameter ln = 790.0000n      ***
1.80000      20.0234u
*****
* hw2_2_2_11.sp
*** parameter ln = 800.0000n      ***
1.80000      19.8142u
```

when Ln parameter **ln** = 0.79u, id is closest to 20uA (20.0234u A)

PMOS

```
* hw2_2_2_11.sp
*** parameter wp = 1.6100u      ***
1.80000      -19.9563u
*****
* hw2_2_2_11.sp
*** parameter wp = 1.6200u      ***
1.80000      -20.0835u
```

when Wp parameter **wp** = 1.61u, id is closest to 20uA (-19.9563u A)

Result

nmos W = 0.25u L = 0.79u

pmos W = 1.61u L = 0.18u

```
* HW2_2_2_11_dc.sp
*-----
.lib 'cic018.1' tt
.temp 27
.option post

*-----
* Simulation netlist
*-----
```



```
Vg g gnd
*Vd d gnd 0.9
Vdd ndd gnd 1.8
```

```
MN1 d g gnd gnd N_18 W=0.25u L=0.79u
MP1 d g ndd ndd P_18 W=1.61u L=0.18u
```

```
*-----
* Stimulus
*-----
```

```
.dc Vg 0 1.8 0.01
.op
.end
```

