

## Homework 4

NYCU EE 112511210 黃仲璿

For detailed method, see hw2.

MN1 d g gnd gnd N\_18 W=250

Unit Inverter (with  $V_d = 1$ )

### 1.1 Design

- \* Assumpti
- \* lib = ci

```

2. L=0.18um

.lib 'c:\ic801.1' tt
.temp 27
.option post

-----
Simulation metlist
-----
Vg g gnd 0.9
Vd d gnd 0.9
Vdd vdd gnd 1.8

M11 d g gnd M_18 W=250n L=900n M=1
M1 d g ndd ndd_p_18 W=250n L=270n M=2

-----
Stimulus
-----
.option captab=1 * nodal capacitance table
.op
.end

2 Capacitance

-----
Result
-----
M11_d_1_0.op.liis

nodal capacitance table
node      = cap
d          = 1.2573f

```

```
* element mn1
* model n_18.1
* id 10.0246u
```

- Method 1:  

```
option captab=1
.op
```
- Method 2:  

```
.dc vg 0 1.8 0.01
.meas dc cg find cap(g) at=0.9
```

- Method 3:

- ```
.dc vg 0 1.8
.print Cmn1=
.print Cmn1=
```

and then use avanw


AvanWaves B-2008.09-SP1 (200811)

File Edit View Window Configuration

File Edit View Window Configuration

- |              |       |
|--------------|-------|
| 100% 30.0000 | 3.00V |
| 100% 30.0000 | 3.00V |
| 100% 30.0000 | 3.00V |

|      |       |
|------|-------|
| 0.4M | ..... |
| 0.6M | ..... |
| 0.8M | ..... |
| 1.0M | ..... |
| 1.2M | ..... |
| 1.4M | ..... |
| 1.6M | ..... |
| 1.8M | ..... |
| 2.0M | ..... |

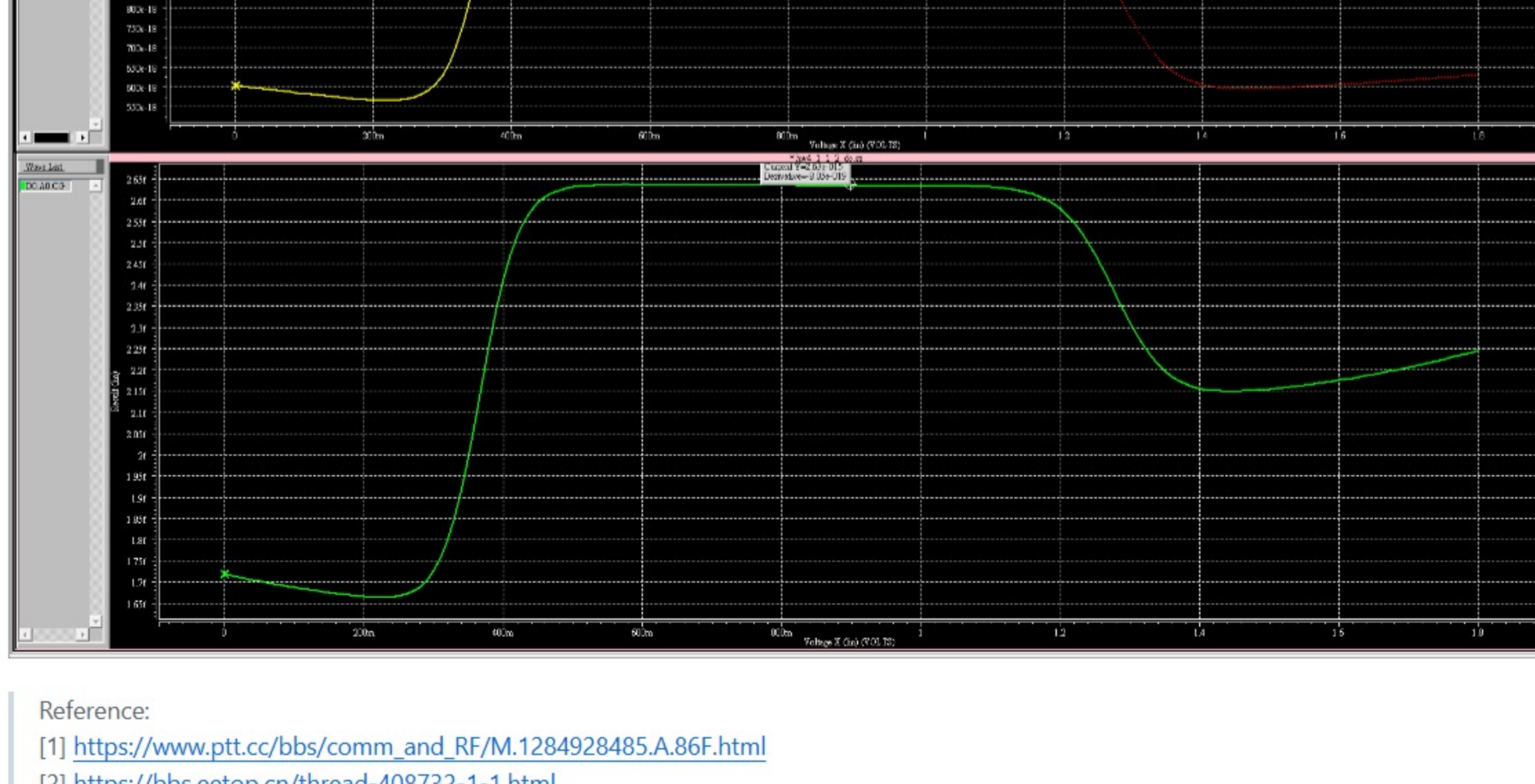


Inverte

- Calculate by hand and then run HSPICE transient simulation.

$V_{o1}$  4  $V_{o2}$

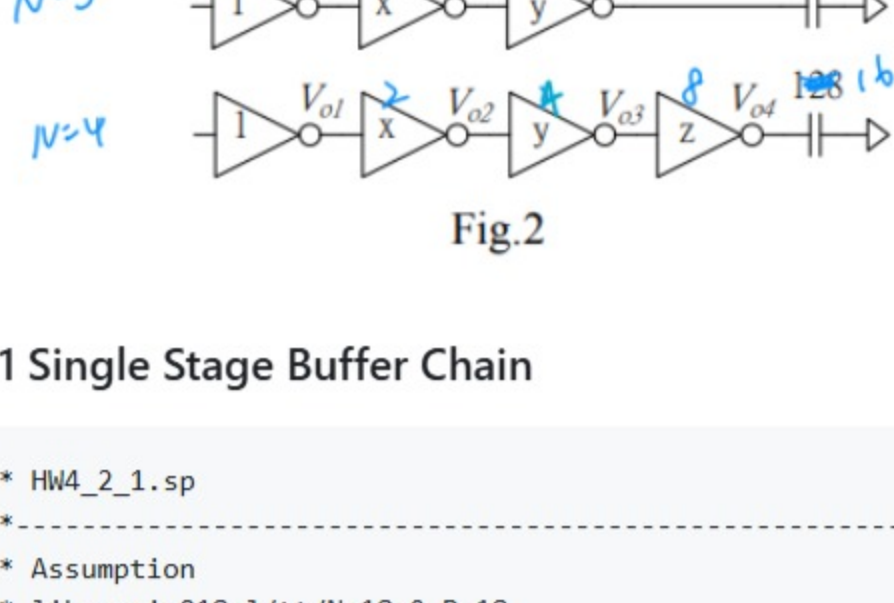$V_{in}$   $V_{out}$   $2.52^\circ$   $6.35^\circ$   $128.16$



576

$\gamma = J/\hbar \approx 2$

- \* 1. temp 27
- \* 2. L=0.18um

```

.lib 'cic808.1' tt
.temp 27
.option post

-----
* Simulation netlist
* Trapezoidal Pulse Source, Page 189, HSPICE® User Guide: Simulation and Analysis
Vxxx n+ n- PULSE [ ([v1 v2 [td [tr [tf [pw [per]]]]) ] ] ]
-----
Vdd nnd gnd 1.8
Vin in gnd PULSE(Bv 1.8V 10ns 0.01ns 0.01ns 19.99ns 60ns)

NM1 o1 in gnd gnd N_18 W=250n L=900n M=1
NM1 o1 in nnd nnd p_18 W=250n L=270n M=2

-----
* 16x inverter load
NM1 n01 in gnd gnd N_18 W=250n L=900n M=16
NM1 n01 in nnd nnd p_18 W=250n L=270n M=32

-----
* Stimulus 250MHz/40ns
* Performing Basic cell Measurements, Page 64B, HSPICE® User Guide: Simulation and Analysis
vtran lps 60ns


.MEAS TRAN Trise TRIG V(o1) val=0.18 TD=10n RISE=1 TARG V(o1) val=1.62 RISE=1
.MEAS TRAN Trfall TRIG V(o1) val=1.62 TD=10n FALL=1 TARG V(o1) val=0.18 FALL=1
.MEAS TRAN Tdelay TRIG V(in) val=0.9 TD=10n RISE=1 TARG V(o1) val=0.9 FALL=1

.print tran v(in) v(o1)
.end

-----
* Result
-----
trise= 1.2633E-09
tfall= 1.7268E-09
tdelay= 7.9930E-10

-----

```

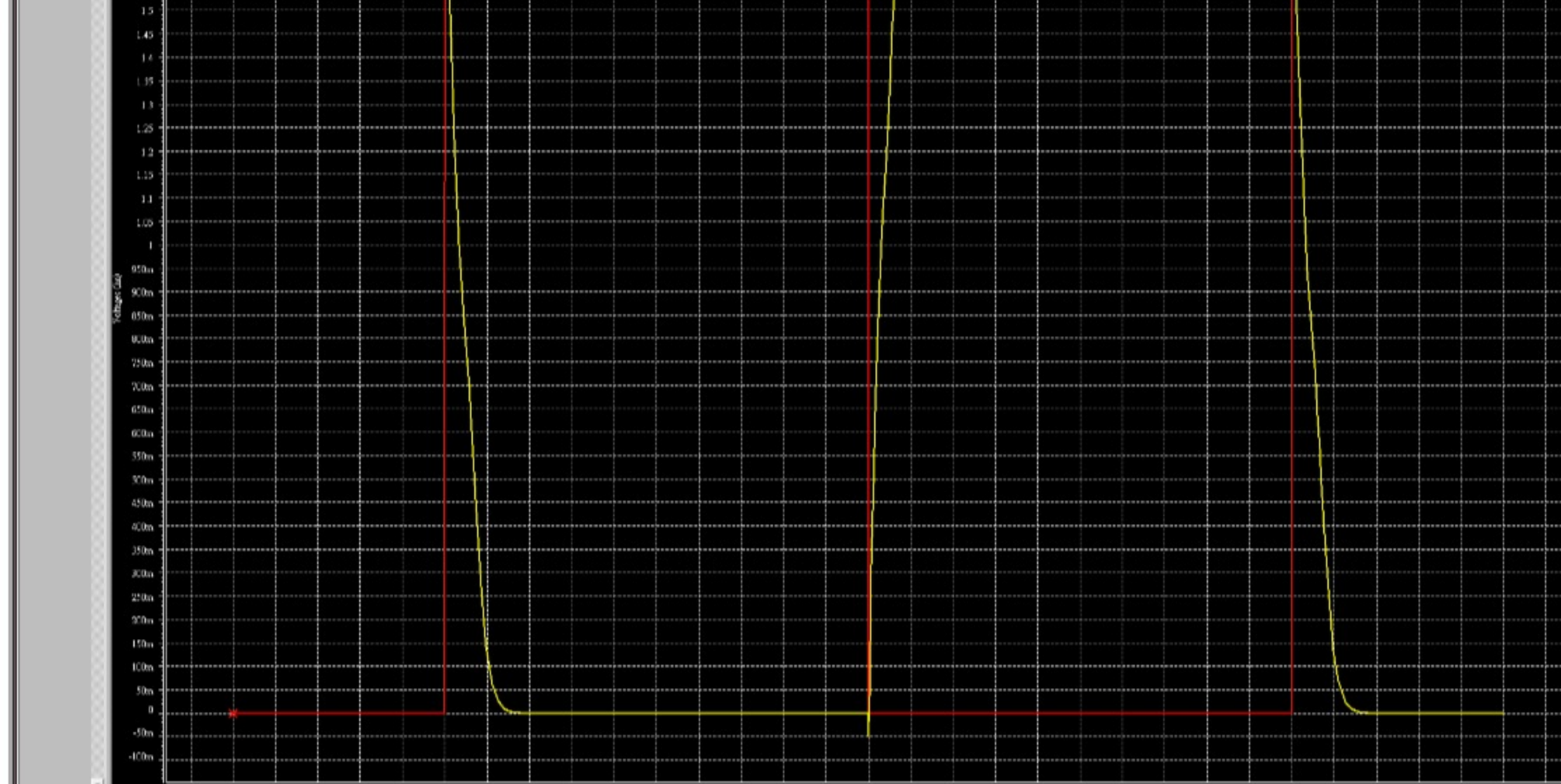

## 2.2 Two Stage Buffer Chain

```

* H04_2_2.sp
-----
Assumption
* lib = cic018.1/tt/tl/l_18 & P_18
* 1. temp 27
* 2. L=0.18um
-----

.lib 'cic018.1' tt
temp 27
.option post

-----
Simulation netlist
Trapezoidal Pulse Source, Page 189, HSPICE® User Guide: Simulation and Analysis
Vxxx n- n- PUL[SE] [(v1 v2 [td [tr [tf [pw [per]]]]]) ()]

Vdd ndd gnd 1.8
Vin in gnd PULSE(0v 1.8v 10ns 0.01ns 0.01ns 19.99ns 40ns)

NM1 o1 in gnd gnd N_18 M=250n L=900n M=1
NP1 o1 in ndd ndd p_18 M=250n L=270n M=2

NM2 o2 o1 gnd gnd N_18 M=250n L=900n M=4
MP2 o2 o1 ndd ndd p_18 M=250n L=270n M=8

* 16x inverter load
NM1 nd o2 gnd gnd N_18 M=250n L=900n M=16
NP1 nd o2 ndd ndd p_18 M=250n L=270n M=32
-----

Stimulus 250Hz/40ns
Performing Basic Cell Measurements, Page 648, HSPICE® User Guide: Simulation and Analysis

tran tps 60ns

MEAS TRAN Trise TRIG V(o2) val=0.18 TD=10n RISE=1 TARG V(o2) val=1.62 RISE=1
MEAS TRAN Tfall TRIG V(o2) val=1.62 TD=10n FALL=1 TARG V(o2) val=0.18 FALL=1
MEAS TRAN Tdelay TRIG V(in) val=0.9 TD=10n RISE=1 TARG V(o2) val=0.9 RISE=1

.print tran v(in) v(o2)
.end


-----
Result
-----
trise= 4.8475E-10
tfall= 5.5330E-10
tdelay= 5.1425E-10
-----

PowerPacB-6-2005.09.01 (20051014)
Date: Sat, 20 May 2006 10:00:00 GMT
By: Ray

[Plot] [Zoom] [Fit] [Print] [Help] [Quit]

-----
Unit: 1.000000
Time: 0.000000
Voltage: 0.000000
Current: 0.000000
Power: 0.000000
-----


```

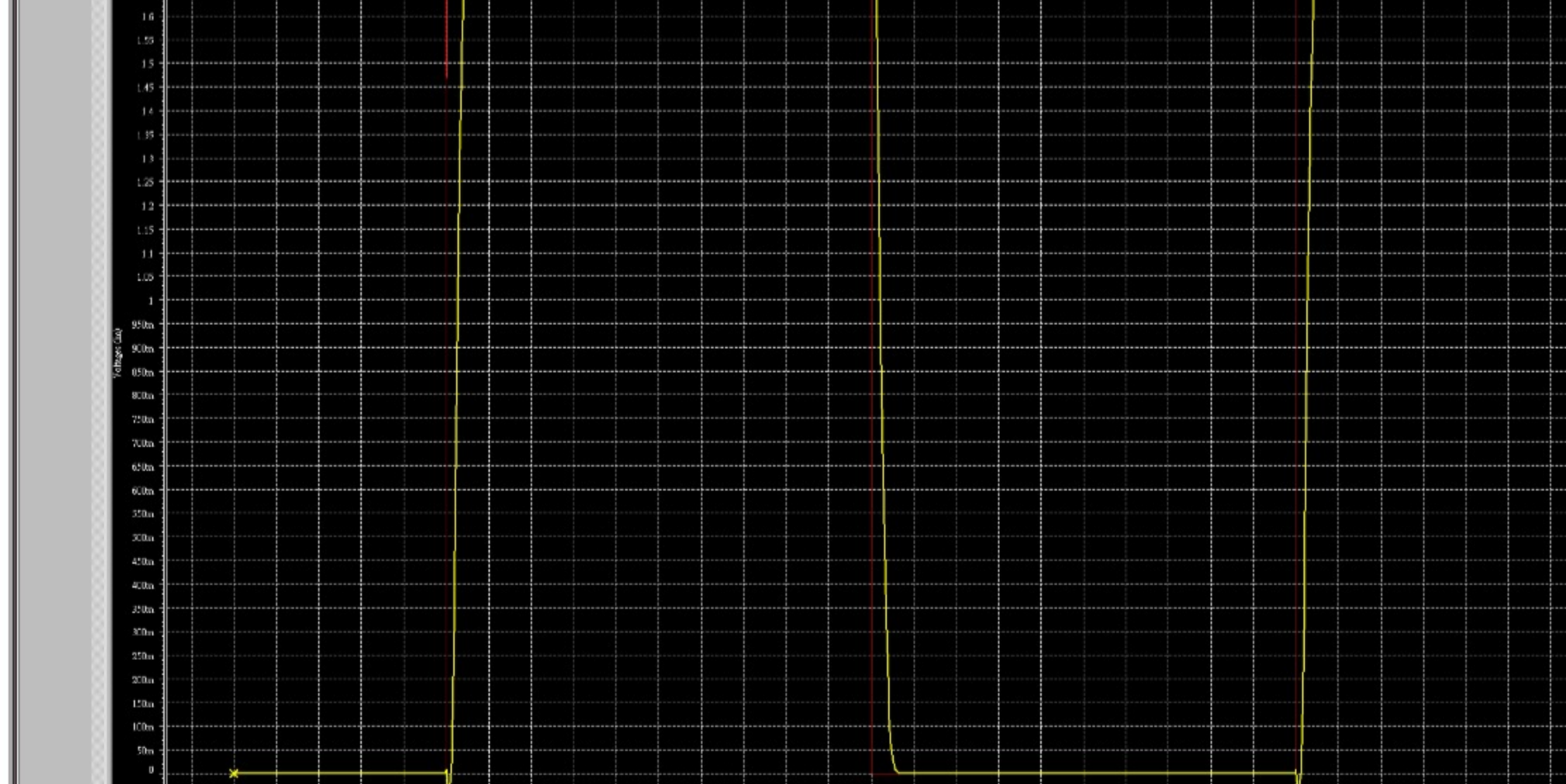

```
Three Stage Buffer Chain
```

```
* HMM_2_3.sp  
-----  
* Assumption  
lib = cic018.1/tt/N_18 & P_18  
    1. temp 27  
    2. L=0.18um  
-----  
.lib "cic018.1" tt  
temp 27  
option post  
  
-----  
Simulation netlist  
Triposical Pulse Source, Page 189, HSPICE® User Guide: Simulation and Analysis  
Vxxx n+ -n- PU[LSE] [[v1 v2 [vd [tr [tf [pw [per]]]]]] []]  
-----  
Vdd nnd gnd 1.8  
Vin in ddr PULSE(0bv 1.8v 10ns 0.01ns 0.01ns 19.99ns 60ns)  
  
* W/L from HMM2  
NMN1 o1 in gnd gnd N_18 W=250n L=900nm M=-1  
MP1 o1 in nnd nnd p_18 W=250n L=270n M=-2  
  
NM2 o2 o1 gnd gnd N_18 W=630n L=900nm M=1 * x2.52  
MP2 o2 o1 nnd nnd p_18 W=630n L=270n M=2 * x2.52  
  
MO3 o3 o2 gnd gnd N_18 W=1590n L=900nm M=1 * x2.52  
MP3 o3 o2 nnd nnd p_18 W=1590n L=270n M=2 * x2.52  
  
* 16x Inverter Load  
NMNL nd o2 gnd gnd N_18 W=250n L=900nm M=-16  
MPL nd o2 nnd nnd p_18 W=250n L=270n M=-16  
  
-----  
Stimulus 25MHz/40ms  
Performing Basic Cell Measurements, Page 648, HSPICE® User Guide: Simulation and Analysis  
  
tran tps 60ns  
  
.MEAS TRAN Trise TRIG V(o3) val=-0.18 TD=10n RISE=1 TARG V(o3) val=-1.62 RISE=1  
.MEAS TRAN TrFall TRIG V(in) val=-1.62 TD=10n FALL=1 TARG V(o3) val=-0.18 FALL=1  
.MEAS TRAN TdDelay TRIG V(in) val=-0.9 TD=10n RISE=1 TARG V(o3) val=-0.9 FALL=1  
  
*.print tran v(in) v(o3)  
.end  
  
-----  
Result  
-----  
trise= 1.8406E-10  
trfall= 1.8691E-10  
tdelay= 6.1823E-10  
  
-----  
Downloaded by 2008/06/01 12:00:14:16  
D:\Data_Series\Herm_Compactos\Joh_Bay  
-----  
[m] [v] [A] [W] [f] [Hz] [kHz] [MHz] [GHz]
```
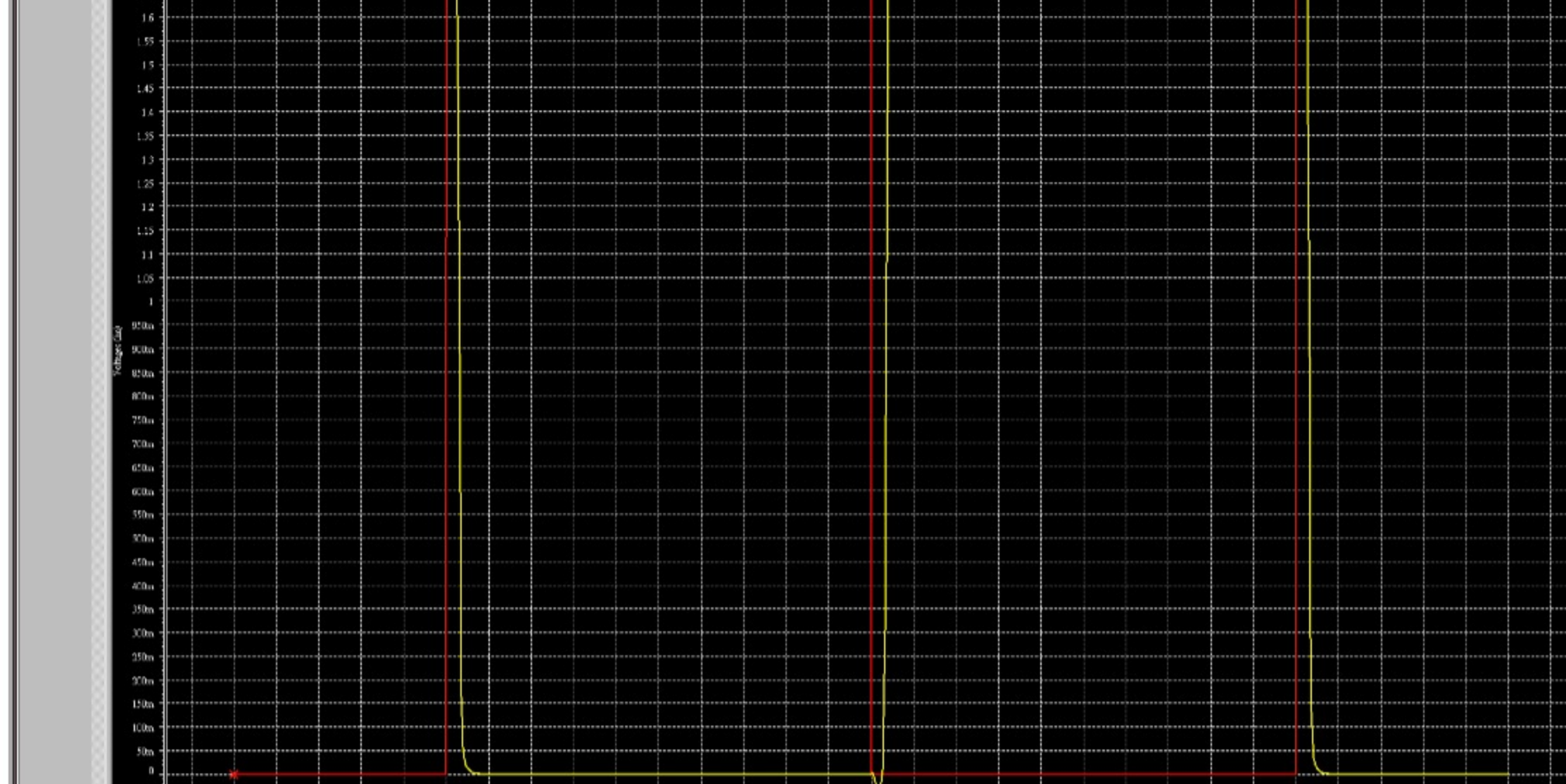
```
Legend:  
trise  
trfall  
tdelay
```



```

**** Four Stage Buffer Chain ****

HWA_2_4.sp
-----
* Assumption
lib = cic018.1/tt/N_18 & P_18
1. temp 27
2. L=0.18um
-----

lib "cic018.1" tt
temp 27
option post
-----

Simulation netlist
Trapezoidal Pulse Source, Page 189, HSPICE® User Guide: Simulation and Analysis
Vxxx n+ n- P[ULSE] [(V1 v2 [td [tr [tf [pw [per]]]])] ()]

Vdd nnd gnd 1.8
Vin in gnd PULSE(0v 1.8v 10ns 0.01ns 0.01ns 19.99ns 40ns)

* N/L from Hw2
M1 W1 o1 in gnd gnd N_18 W=250n L=900n M=1
M1 o1 in nnd nnd p_18 W=250n L=270n M=2

M2 o2 o1 gnd gnd N_18 W=250n L=900n M=1
M2 o2 o1 nnd nnd p_18 W=250n L=270n M=4

M3 o3 o2 gnd gnd N_18 W=250n L=900n M=4
M3 o3 o2 nnd nnd p_18 W=250n L=270n M=8

M4 o4 o3 gnd gnd N_18 W=250n L=900n M=8
M4 o4 o3 nnd nnd p_18 W=250n L=270n M=16

* 16x inverter load
N1L nld o4 gnd gnd N_18 W=250n L=900n M=16
N1L nld o4 nnd nnd p_18 W=250n L=270n M=32
-----

Stimulus 250hz/40ns
Performing Basic Cell Measurements, Page 64B, HSPICE® User Guide: Simulation and Analysis

.tran tps 60ns

.REAS TRAN Trise TRIG V(o4) val=0.18 TD=10n RISE=1 TARG V(o4) val=1.62 RISE=1
.REAS TRAN Trfall TRIG V(o4) val=1.62 TD=10n FALL=1 TARG V(o4) val=0.18 FALL=1
.REAS TRAN Tdelay TRIG V(in) val=0.9 TD=10n RISE=1 TARG V(o4) val=0.9 RISE=1

.print tran v(in) v(o4)
.end
-----

* Result
trise= 2.6542E-10
trfall= 1.2837E-10
tdelay= 6.6552E-10

```

